

# Resistance



NAME: \_\_\_\_\_

Complete the following assignment:

1. What is resistance?

2. What is a resistor?

3. Would a resistor be a poor conductor or a good conductor?

4. What is the unit and symbol for resistance?

5. When reading colour bands of a carbon resistor, how do you know which end to start reading from?

6. Describe the purpose of each band on a carbon resistor:

- a) 1<sup>st</sup> band
- b) 2<sup>nd</sup> band
- c) 3<sup>rd</sup> band
- d) 4<sup>th</sup> band

7. A resistor has a ohm-rating of  $100 \Omega$ . What would the possible range of resistance if the resistor had a:

- a) Gold band: \_\_\_\_\_ to \_\_\_\_\_
- b) Silver band: \_\_\_\_\_ to \_\_\_\_\_
- c) No 4<sup>th</sup> band: \_\_\_\_\_ to \_\_\_\_\_

8. How would current change in a circuit where a  $1000 \Omega$  resistor is replaced by a  $10 \Omega$  resistor?

9. Determine the resistance of a resistor with the following bands:

- a) blue, green, brown: \_\_\_\_\_  $\pm$  \_\_\_\_\_
- b) yellow, white, black, gold: \_\_\_\_\_  $\pm$  \_\_\_\_\_
- c) red, yellow, orange, silver: \_\_\_\_\_  $\pm$  \_\_\_\_\_

10. The following appliances all run on a 120 V circuit. Based on the current draw of each appliance, arrange the appliances from greatest to least resistance:

Appliance	Kettle	T.V.	Toaster	Microwave	Light Bulb
Current Draw (A)	12	1.7	8.3	5	0.8


**Highest Resistance**

- (1) \_\_\_\_\_
- (2) \_\_\_\_\_
- (3) \_\_\_\_\_
- (4) \_\_\_\_\_
- (5) \_\_\_\_\_

**Lowest Resistance**
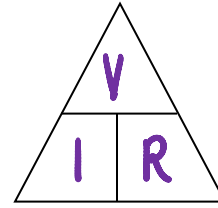
# OHM'S LAW PROBLEMS

Complete the following questions. Show all work.



1. What current will flow through a wire of  $2\ \Omega$  resistance, connected to a  $6\ \text{V}$  automobile battery?
2. What voltage is necessary to cause a current of  $2\ \text{A}$  through a wire of  $40\ \Omega$  resistance?
3. A wire whose resistance is  $3\ \Omega$  is connected to the poles of a storage battery and the voltage between the ends of the wire is  $6\ \text{V}$ . What is the current in the wire?
4. The resistance of an electric iron is  $20\ \Omega$  and the current through it is  $6\ \text{A}$ . What is the voltage of the heater coil in the iron?
5. The current through a  $60\ \text{watt}$  lamp is  $0.5\ \text{A}$  and the voltage between the ends of the filament wire is  $120\ \text{V}$ . What is the resistance of the filament in the lamp?
6. If the current through the filament of an automobile's tail-light is  $3\ \text{A}$  and the resistance of the filament is  $2\ \Omega$ , what is the voltage between the ends of the filaments?

7. What is the current through a  $20\ \Omega$  resistor with a  $6\text{V}$  potential across it?
  
  
  
  
  
  
  
  
  
  
8. What is the potential difference (voltage) across a  $25\ \Omega$  resistor if the current flowing through it is  $25\ \text{A}$ ?
  
  
  
  
  
  
  
  
  
  
9. What is the resistance of a circuit in which a  $100\ \text{V}$  battery produces a  $12\ \text{A}$  current?
  
  
  
  
  
  
  
  
  
  
10. A carbon resistor permits  $0.3\ \text{mA}$  current to run through it when the potential difference across it is  $5000\ \text{V}$ . What is the resistance?
  
  
  
  
  
  
  
  
  
  
11. What is the voltage drop (voltage at a particular point) across a  $15\ 000\ \Omega$  resistor if the current through it is  $0.0025\ \text{A}$ ?
  
  
  
  
  
  
  
  
  
  
12. How much current will run through a  $25\ \text{M}\Omega$  resistor with  $10\ 000$  volts across it?