

$$V = IR$$

Worksheet: Complex Circuit Problems, Ep.905

Name Key

$$\frac{1}{30} + \frac{1}{30} = \frac{2}{30}$$

$$= \frac{1}{15} \rightarrow 15\Omega$$

$$15\Omega + 5\Omega = 20\Omega$$

